

Enrolment No:.....

Name of Student.....



BENNETT
UNIVERSITY
THE TIMES GROUP

NAAC
GRADE A+
ACCREDITED UNIVERSITY

End Semester Examinations, May 2026

Even Semester 2025-26

B.Tech. (CSE)/ B.Tech. (CSE- Global) – 2nd Semester

2025CSET151- INTRODUCTION TO ELECTRICAL & ELECTRONICS ENGINEERING

Time: 2 hrs.

Max Marks: 40

Note: *Student must attempt 5 Questions in total. First question is compulsory, and student must attempt questions from each section. Marks are indicated against each question. Use of non-programmable scientific calculator is allowed.*

PART-A

Attempt any 6 questions from out of eight.

2*6=12 Marks

- Q.1 (a) State the maximum power transfer theorem of electrical networks. [CO-1] [L-1] 2
(b) Calculate the equivalent resistance between the terminals *a-b* for the electrical circuit shown in Fig. 1. [CO-1] [L-3] 2

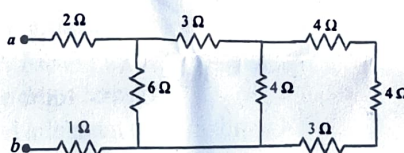


Fig. 1

- (c) Explain the input-output relationship of the R-L high pass filter. [CO-2] [L-1] 2
(d) Explain the operation of the Zener Diode as a voltage regulator using the appropriate circuit diagram. [CO-3] [L-1] 2
(e) Write the P-N junction diode current equation and explain the variables. [CO-3] [L-2] 2
(f) At what reverse bias voltage does the reverse bias current in a PN Junction reaches 90% of its reverse saturation current? [CO-3] [L-3] 2
(g) Define common mode rejection ratio (CMRR) of the Op-Amp and what is CMRR value of an ideal Op-amp. [CO-4] [L-2] 2
(h) Explain virtual short (virtual ground) concept of the Operational Amplifier along with the circuit diagram. [CO-4] [L-] 2

PART-B

Attempt any 2 questions from this part B.

- Q.2 Using nodal analysis, find V_0 in the circuit of Fig. 2.

[CO-1] [L-4] 6

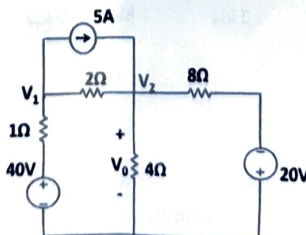


Fig. 2

Q.3 For the diode circuit shown in Fig. 3, $V_S = 2$ V. The silicon diode has a reverse saturation current of 1 nA at 300 K. Given that $V = 0.7$ V. Assume ideality factor=1.

- Find R_2 when $R_1 = 1$ k Ω
- Find R_1 when $R_2 = 1$ k Ω

[CO-3] [L-3] 6

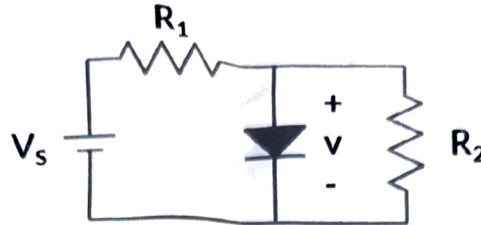


Fig. 3

Q.4 Consider a summing amplifier shown in Fig. 4. Given that $R_1 = 1$ k Ω , $R_2 = 1.5$ k Ω , $R_3 = 2$ k Ω , and $R_F = 10$ k Ω . If $V_{I1} = 0.5$ V, $V_{I2} = 0.75 \sin(60\pi t)$ and $V_{I3} = 1.0 \sin(30\pi t)$, find the output voltage?

[CO-4] [L-3] 6

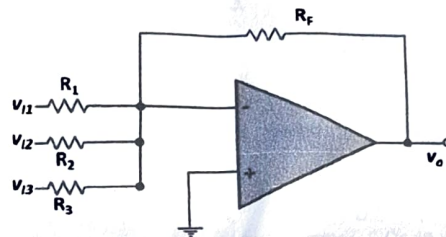


Fig. 4

6*2=12 Marks

PART-C

Q.5 For the circuit shown in Fig. 5, identify the filter type, find the transfer function and cut-off frequency of the filter. The output of the filter is taken between nodes C and D.

[CO-2] [L-3] 8

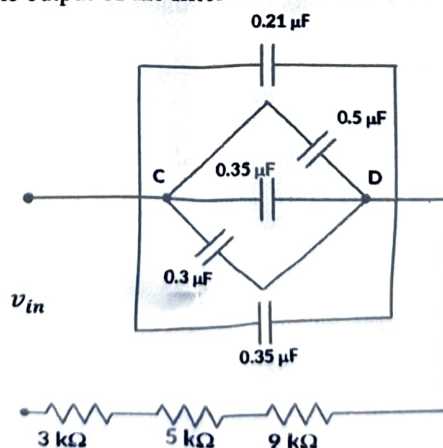


Fig. 5

OR

For the circuit shown in Fig. 6, identify the filter type, find the transfer function and cut-off frequency of the filter. The output of the filter is taken between nodes C and D. [CO-2] [L-3] 8

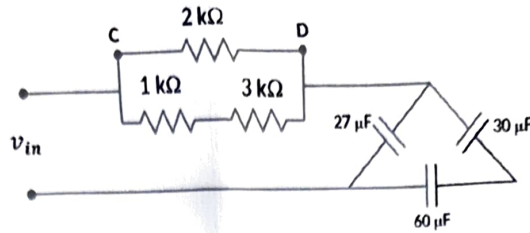


Fig. 6

Q.6 For the diode circuit (Si diodes with cut in voltage of 0.6 V) shown in Fig. 7, let $R_f = 1 \text{ k}\Omega$ and $R = 9 \text{ k}\Omega$. Find the output voltage V_0 when

- $V_1 = V_2 = 0 \text{ V}$
- $V_1 = 10 \text{ V}, V_2 = 0 \text{ V}$
- $V_1 = V_2 = 10 \text{ V}$

[CO-3] [L-4] 8

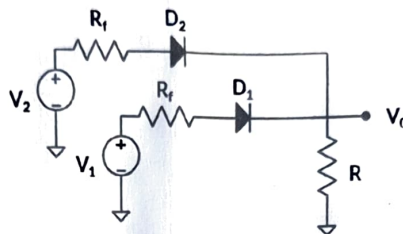


Fig. 7

OR

Consider the circuit shown in Fig. 1. Given that, $R = 4 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$ and $V_Z = 30 \text{ V}$. The input voltage V_{in} can vary between 70 to 100 V. Answer the following questions.

- What is the range of voltage drops across R ?
- Calculate the maximum and minimum currents through R ?
- What is the current in the load resistor?
- Calculate the maximum and minimum currents through the Zener diode.
- What is the minimum power rating of Zener diode that needs to be used in the circuit?

[CO-3] [L-4] 8

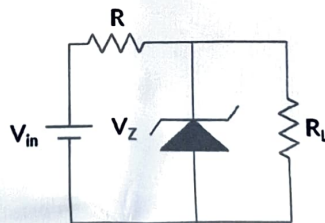


Fig. 8

8*2=16 Marks
